



Power Systems Analysis, L3 2018

Lennart Söder
Professor in Electric Power Systems

Reciprocity theorem



Assume that a voltage source is connected to a terminal a in a linear reciprocal network and is giving rise to a current at terminal b . According to the reciprocity theorem, the voltage source will cause the same current at a if it is connected to b .

Twoport theory

$$\begin{bmatrix} \overline{U}_a \\ \overline{I}_a \end{bmatrix} = \begin{bmatrix} \overline{A} & \overline{B} \\ \overline{C} & \overline{D} \end{bmatrix} \begin{bmatrix} \overline{U}_b \\ \overline{I}_b \end{bmatrix}$$





A reciprocal twoport \Rightarrow

$$\overline{A} \cdot \overline{D} - \overline{B} \cdot \overline{C} = 1$$

Symmetrical twoports \Rightarrow

$$\overline{A} = \overline{D}$$

Model of symmetrical transmission line

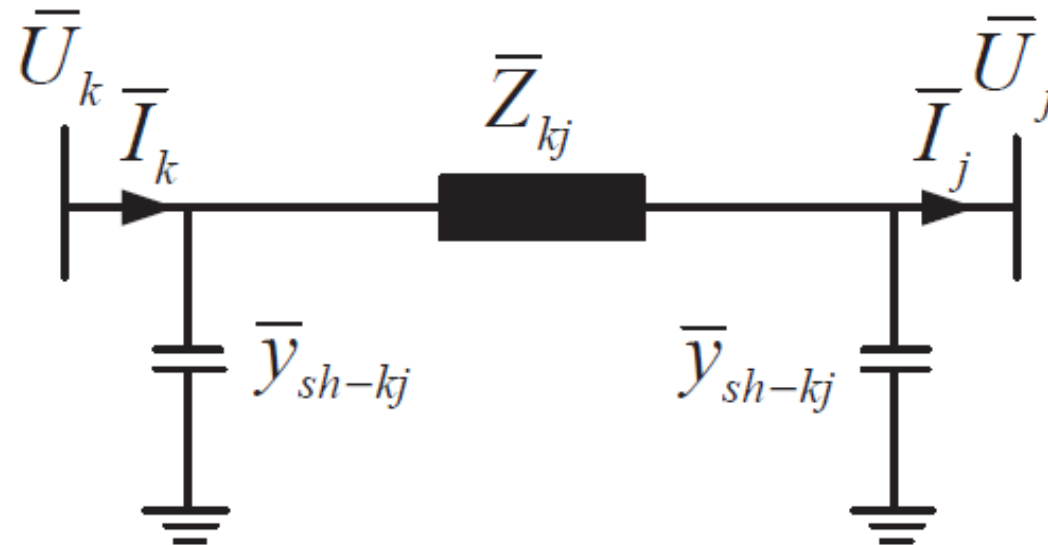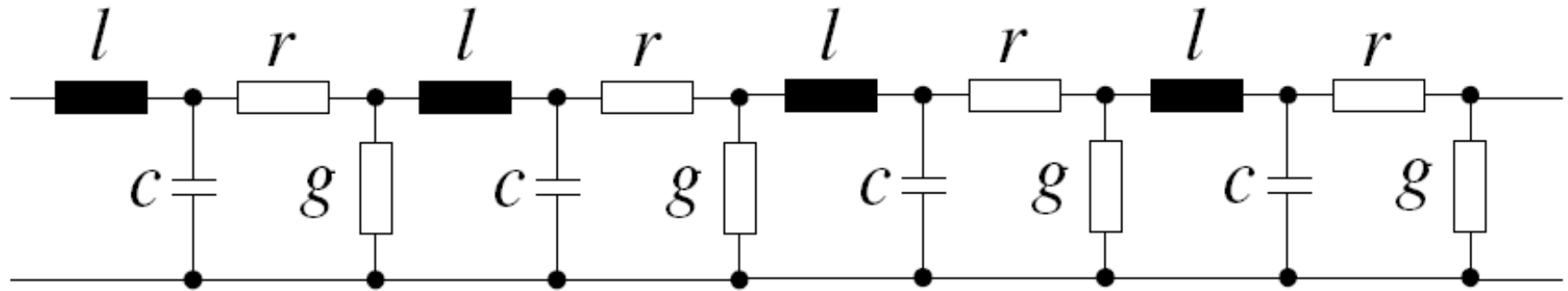

Two port parameters for the line :



$$\begin{bmatrix} \overline{U}_k \\ \overline{I}_k \end{bmatrix} = \begin{bmatrix} \overbrace{1 + \overline{y}_{sh-kj} \cdot \overline{Z}_{kj}}^{\overline{A}} & \overbrace{\overline{Z}_{kj}}^{\overline{B}} \\ \underbrace{\overline{y}_{sh-kj}(2 + \overline{y}_{sh-kj} \cdot \overline{Z}_{kj})}_{\overline{C}} & \underbrace{1 + \overline{y}_{sh-kj} \cdot \overline{Z}_{kj}}_{\overline{D}} \end{bmatrix} \begin{bmatrix} \overline{U}_j \\ \overline{I}_j \end{bmatrix}$$



Two-port parameters for a transformer and a short line $\overline{Y}_{sh-kj} = 0$

$$\begin{bmatrix} \overline{U}_k \\ \overline{I}_k \end{bmatrix} = \begin{bmatrix} 1 & \overline{Z}_{kj} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \overline{U}_j \\ \overline{I}_j \end{bmatrix}$$

Connection to a network

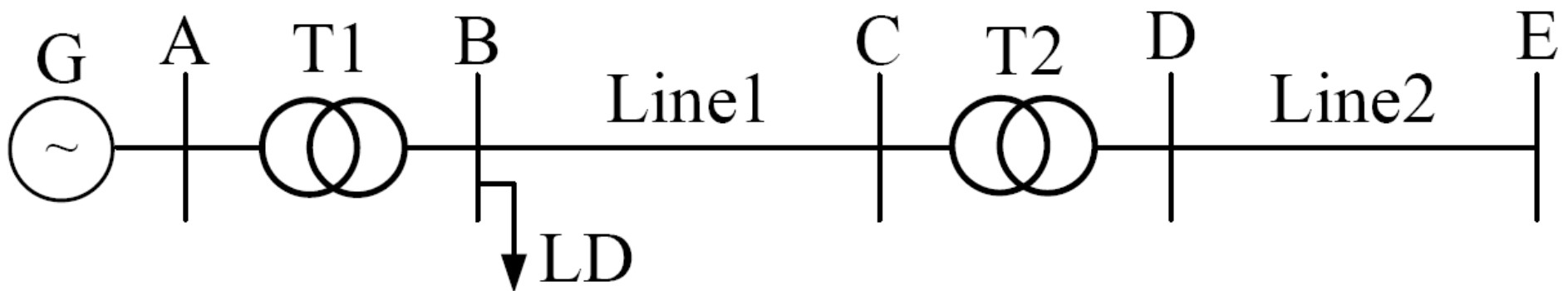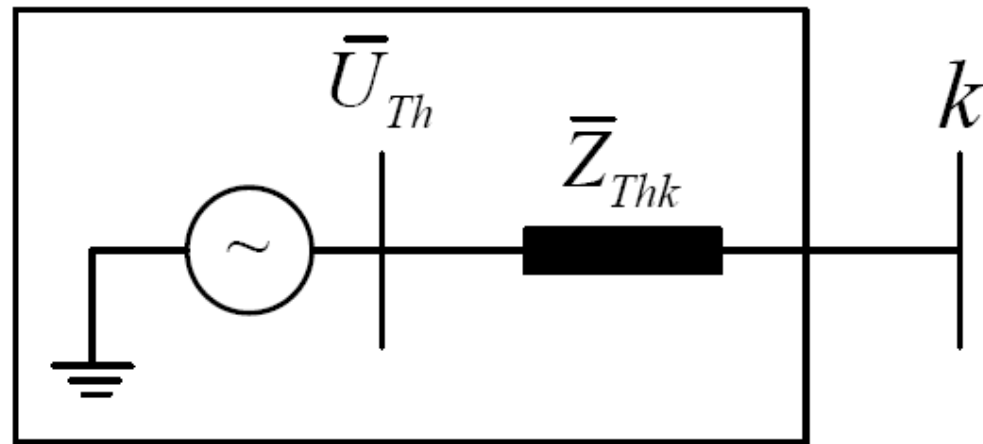


Example 6.1



At a bus with a short circuit capacity of 500 MVA and $\cos\varphi_k = 0$, inductive, an impedance load of 4 MW, $\cos\varphi_{LD} = 0.8$ at nominal voltage, is connected. Calculate the change in bus voltage when the load is connected.


Home Exam S1-S3

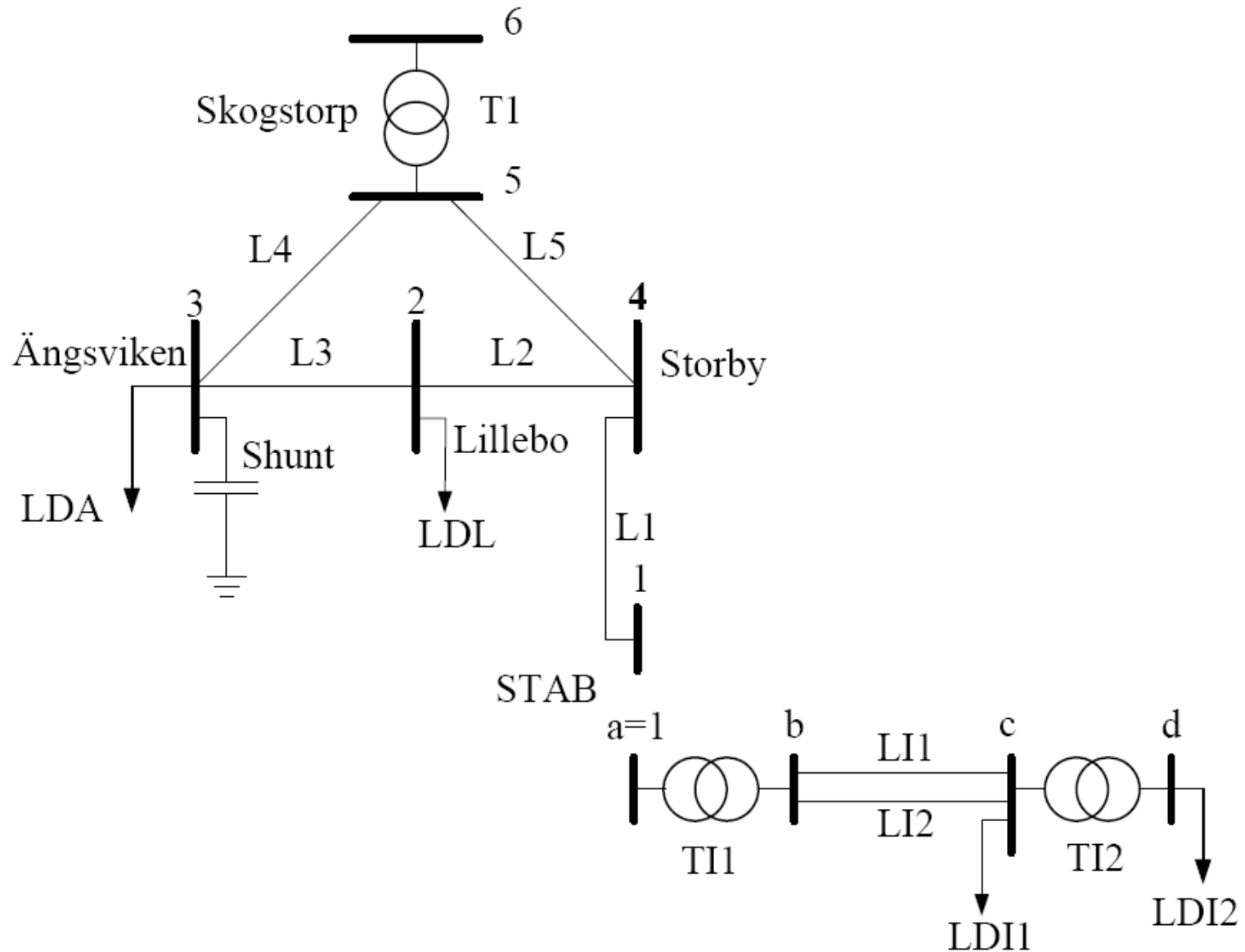

Home Exam S1 (Sept-18)

This assignment is dealing with the electrical network of a factory **fed from** a 40 kV meshed grid. The system data can be found in the Excel file.

Example 6.2

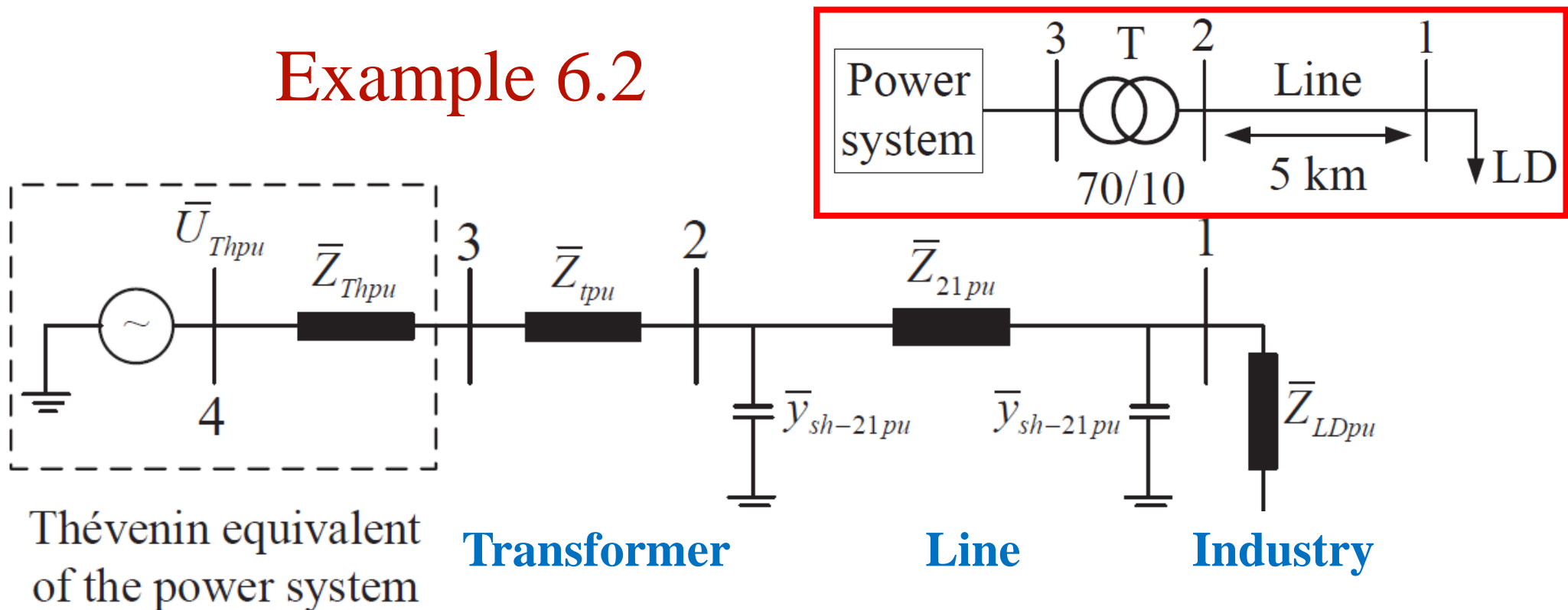

Home Exam S1 (Sept-18), Part 1


- a. Based on the given data, draw the single-line diagram of the electrical network of the factory. **(5%)**
- b. As seen from node **a**, make the two-port model and give the values of the elements of the two-port matrix in pu. **(10%)**
- c. Give the value of the impedance of the entire system in pu. **(10%)**
- d. Assume that the transformer “T11” is fed with nominal voltage. Find the voltage at node **e** in kV. **(20%)**
- e. Find the consumed active power of the load at node **e** in MW, and also its power factor. **(20%)**
- f. Find the total losses in the factory in kW. **(20%)**
- g. Plot the normalized active power consumption at node **e** (based on the obtained active power in task d) when the voltage at node **a** varies from 0.8 to 1.2 pu. **(15%)**

Example 6.2



A small industry is fed by a transformer (5 MVA, 70/10 kV, $x = 4\%$) which is located at a distance of 5 km. The electric power demand of the industry is 400 kW at $\cos\phi=0.8$, lagging, at a voltage of 10 kV. The industry can be modeled as an impedance load. The 10 kV line has a series impedance of $0.9+j0.3 \Omega/\text{phase, km}$ and a shunt admittance of $j3 \cdot 10^{-6} \text{ S}/\text{phase, km}$. Assume that the line is modeled by the II-equivalent. Calculate the voltage level at the industry as well as the power fed by the transformer into the line. When the industry is not connected, a short circuit current of 0.3 kA side of the transformer when a three-phase short circuit is applied at nominal voltage.

Example 6.2

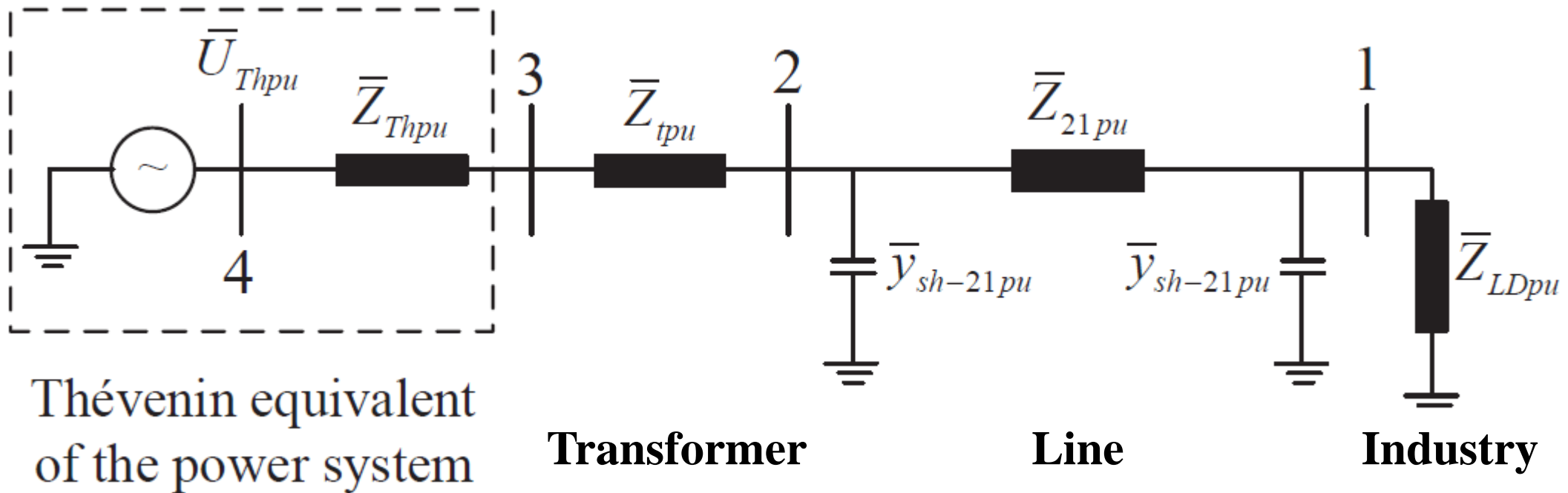

```
clear
```

```
deg=180/pi;
```

```
rad=1/deg;
```

```
%--- Example 6.2
```

```
% Choose the base values
```

```
Sb=0.5; Ub10=10; Ib10=Sb/Ub10/sqrt(3); Zb10=Ub10^2/Sb;
```

```
Ub70=70; Ib70=Sb/Ub70/sqrt(3);
```

```
%Calculate the per-unit values of the Thevenin equivalent of the system
```

```
UTh=70*exp(j*0*rad);
```

```
Isc=0.3*exp(j*-90*rad);
```

```
UThpu =UTh/Ub70;
```

```
Iscpu =Isc/Ib70;
```

```
ZThpu =UThpu/Iscpu;
```

```
% Calculate the per-unit values of the transformer
```

```
Zt=j*4/100;Snt=5;
```

```
Ztpu=Zt*Sb/Snt;
```

```
%Calculate the per-unit values of the line
```

```
Z21pu=5*(0.9+j*0.3)/Zb10;
```

```
ysh21pu=5*(j*3*1E-6)*Zb10/2;
```

```
%Calculate the per-unit values of the industry impedance
```

```
cosphi=0.8;sinphi=sqrt(1-cosphi^2);
```

```
Un=Ub10;PLD=0.4;absSLD=PLD/cosphi;
```

```
SLD=absSLD*(cosphi+j*sinphi);
```

```
ZLDpu=Un^2/conj(SLD)/Zb10
```



```

% The twoport of the system
AL=1+ysh21pu*Z21pu;
BL=Z21pu;
CL=ysh21pu*(2+ysh21pu*Z21pu);
DL=AL;

F_L=[AL BL ; CL DL];
F_Th_tr=[1 ZThpu+Ztpu ; 0 1];
F_tot=F_Th_tr*F_L;


%The impedance of the entire system
Ztotpu=(F_tot(1,1)*ZLDpu+F_tot(1,2))/(F_tot(2,1)*ZLDpu+F_tot(2,2))
I4pu = UThpu/Ztotpu;

%The power fed by the transformer into the line
U2pu_I2pu=inv(F_Th_tr)*[UThpu;I4pu];
S2=U2pu_I2pu(1,1)*conj(U2pu_I2pu(2,1))*Sb

%The voltage at the industry
U1pu_I1pu=inv(F_tot)*[UThpu;I4pu];
U1=abs(U1pu_I1pu(1,1))*Ub10,

```

Admittance matrix - 1

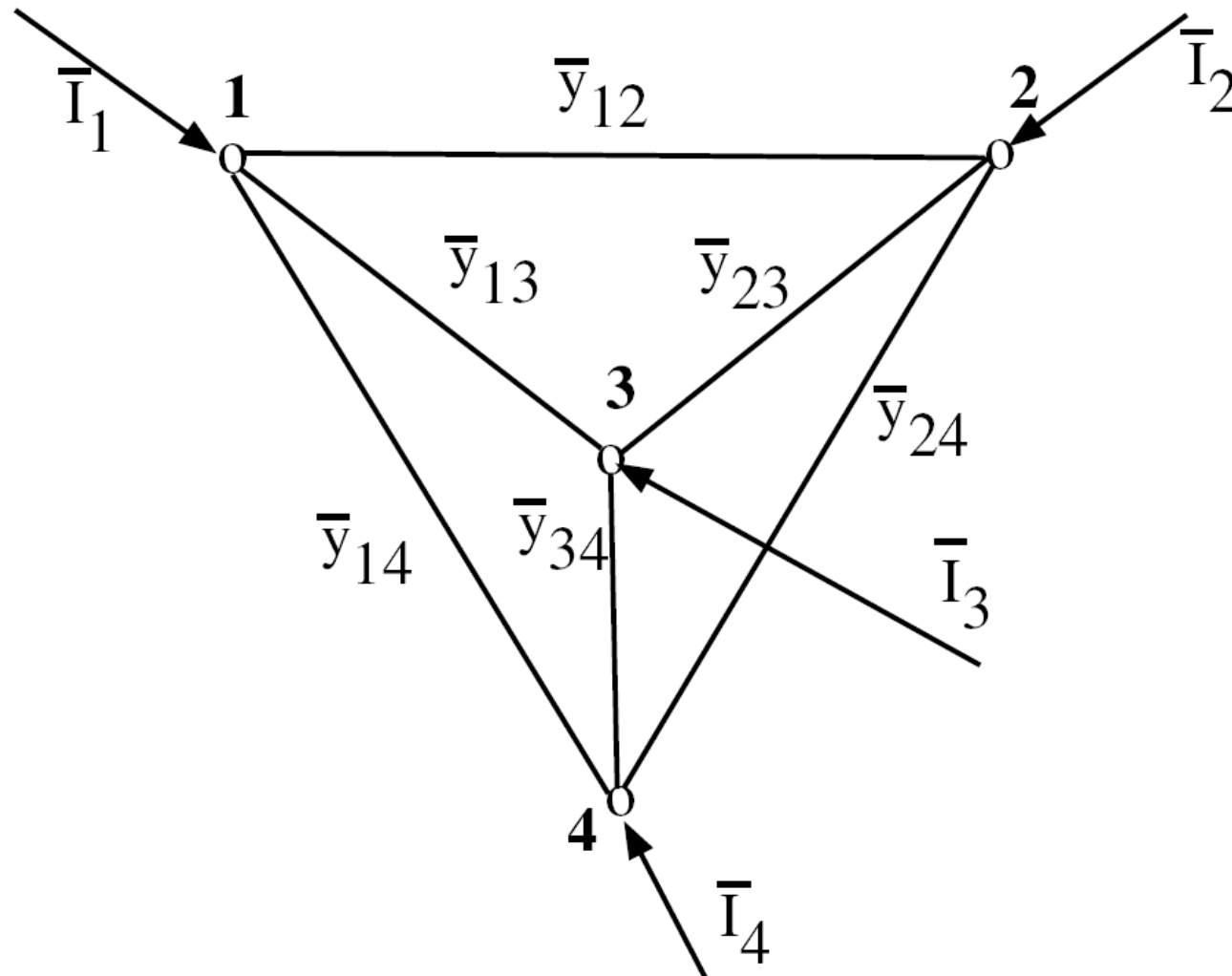


Admittance matrix - 2

For the Y-bus matrix the following properties are valid:

- It can be uniquely determined from a given admittance network.
- The diagonal element Y_{kk} = the sum of all admittances connected to bus k .
- Non-diagonal element $Y_{ik} = -y_{ik}$ where y_{ik} is the admittance between bus i and bus k .
- This gives that the matrix is symmetric, i.e. $Y_{ik} = Y_{ki}$ (one exception is when the network includes phase shifting transformers).
- It is singular since $I_1 + I_2 + I_3 + I_4 = 0$



Millman's theorem - 1

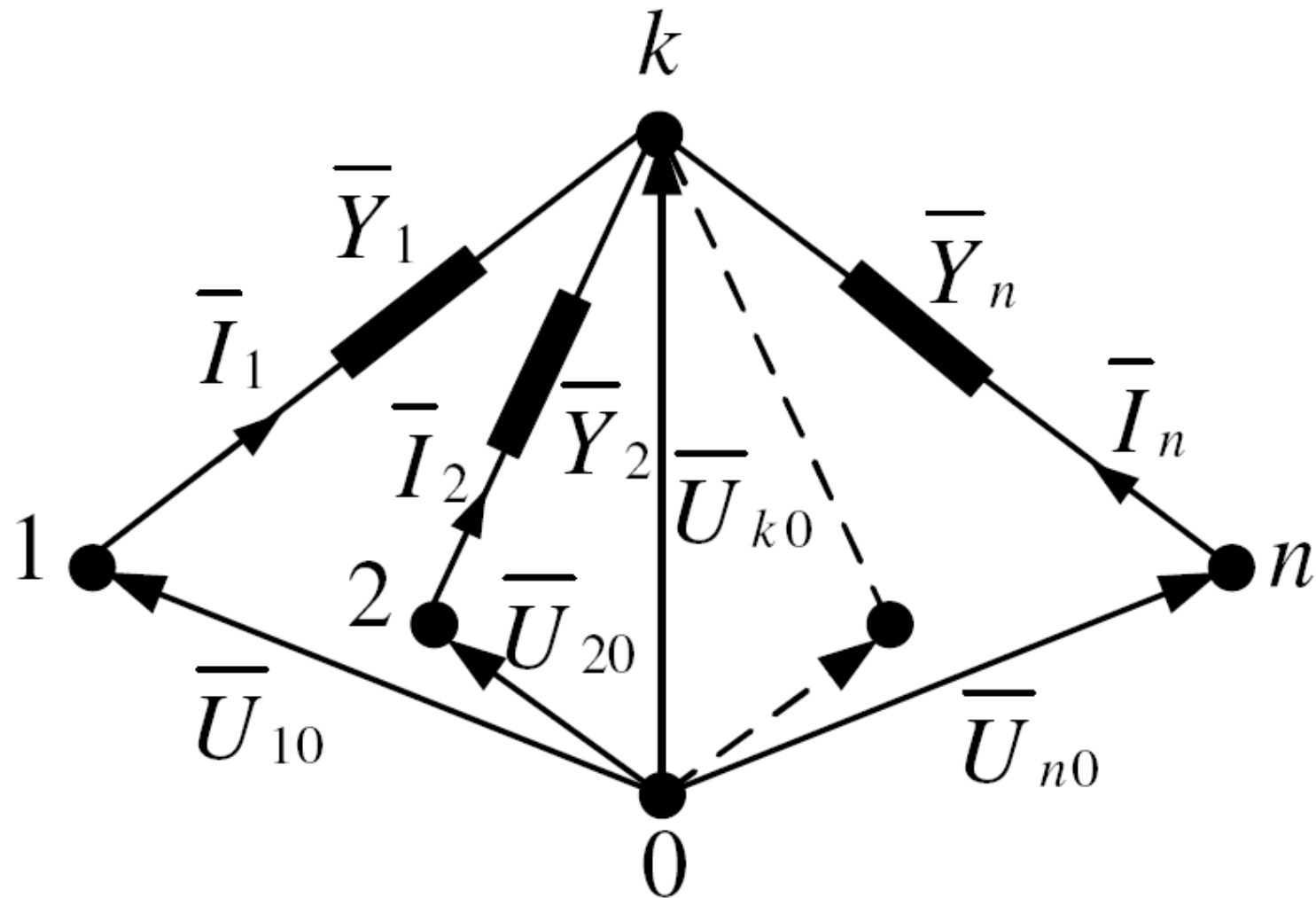

Millman's theorem - 2

The Y-bus matrix for this network can be formed as




$$\begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \vdots \\ \bar{I}_n \\ \bar{I}_k \end{bmatrix} = \begin{bmatrix} \bar{Y}_1 & 0 & \dots & 0 & -\bar{Y}_1 \\ 0 & \bar{Y}_2 & \dots & 0 & -\bar{Y}_2 \\ \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & \dots & \bar{Y}_n & -\bar{Y}_n \\ -\bar{Y}_1 & -\bar{Y}_2 & \dots & -\bar{Y}_n & (\bar{Y}_1 + \bar{Y}_2 + \dots + \bar{Y}_n) \end{bmatrix} \begin{bmatrix} \bar{U}_{10} \\ \bar{U}_{20} \\ \vdots \\ \bar{U}_{n0} \\ \bar{U}_{k0} \end{bmatrix}$$



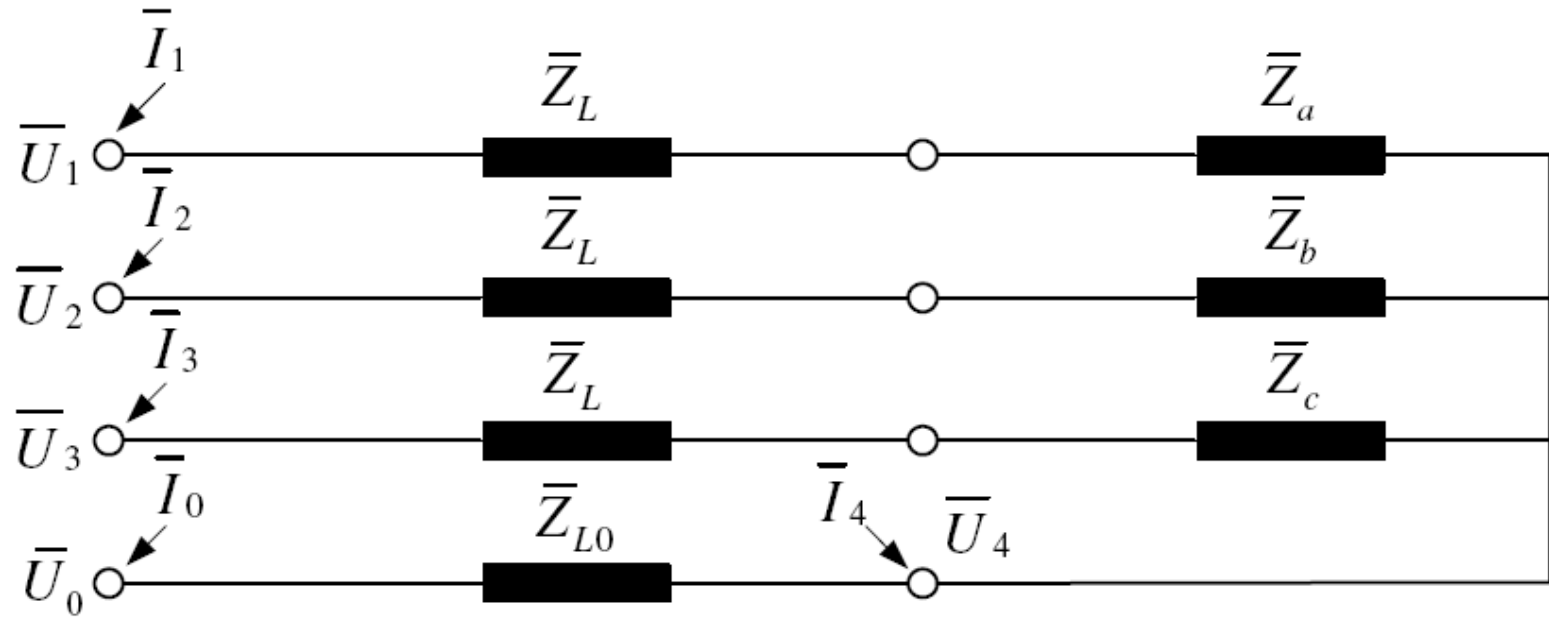Example 5.2

The student Elektra lives in a house situated 2 km from a transformer having a completely symmetrical three-phase voltage ($U_a = 220 \text{ V} \angle 0^\circ$, $U_b = 220 \text{ V} \angle -120^\circ$, $U_c = 220 \text{ V} \angle 120^\circ$). The house is connected to this transformer via a three-phase cable (EKKJ, $3 \cdot 16 \text{ mm}^2 + 16 \text{ mm}^2$). A cold day, Elektra switches on one 1000 W radiator (at 220 V with $\cos\phi = 0.995$ lagging) to phase a, three radiators to phase b and two to phase c. Assume that the cable can be modelled as four impedances connected in parallel ($z_{L0} = 1.15 + j0.08 \text{ } \Omega/\text{phase, km}$, $z_{L0} = 1.15 + j0.015 \text{ } \Omega/\text{km}$) and that the radiators also can be considered as impedances. Calculate the total thermal power given by the radiators.



$$\bar{Z}_L = 2.3 + j0.16 \, \Omega \quad \bar{Z}_{L0} = 2.3 + j0.03 \, \Omega$$

$$\bar{Z}_a = 47.9 + j4.81 \, \Omega, \quad \bar{Z}_b = 15.97 + j1.60 \, \Omega,$$

$$\bar{Z}_c = 23.96 + j2.40 \, \Omega$$